
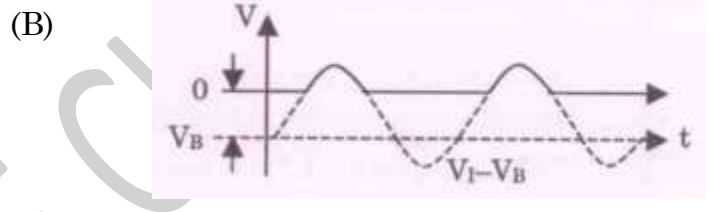
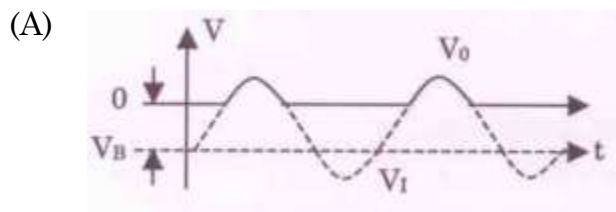


Diode circuits: clipping, clamping and rectifiers

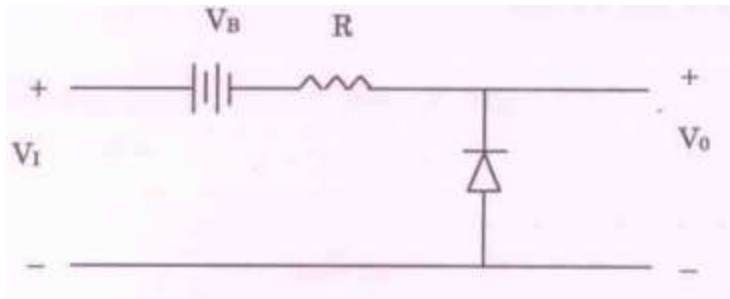Q1. Output response of the diode clipper circuit shown in the figure below will be





(C) Both A and B


(D) None of the above.

(ISRO-2016)

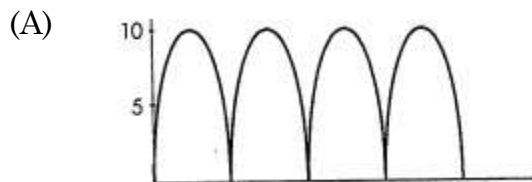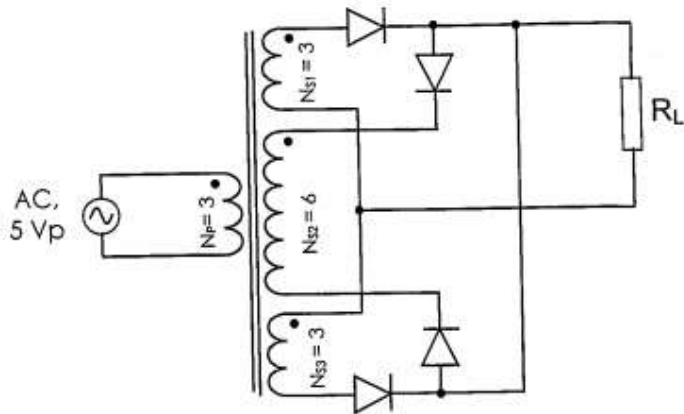
Q2. The diode in the following circuit is ideal. Which is the correct waveform across the R_L ?



(C)

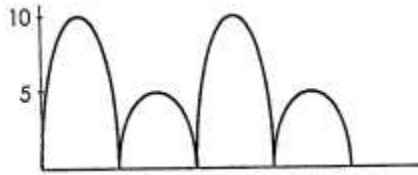

(D)

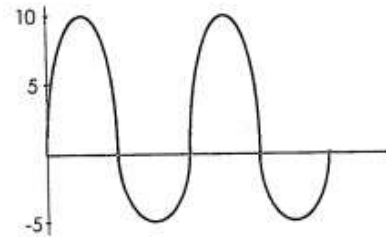

(ISRO-2014)

Q3. In full wave rectifier with center tap transformer, If the voltage between one end of secondary winding and center tap is 300V peak. Then PIV (Peak inverse voltage) is

- (A)300V (B)150V (C)600V (D)900V (ISRO-2012)

Q4. A P-N junction is in series with a 100ohm resistor is forward bias so that the current of 100mA flows. If the voltage across the combination is increased instantaneously reversed to 10V at time $t = 0$ the reverse current that flow through the junction at $t = 0$ is approximately given by


- (A)0mA (B)200mA (C)50mA (D)100mA (ISRO-2011)

Q5. Ripple factor of half wave rectifier is

- (A)1.65 (B)1.45 (C)1 (D)1.21 (ISRO-2011)

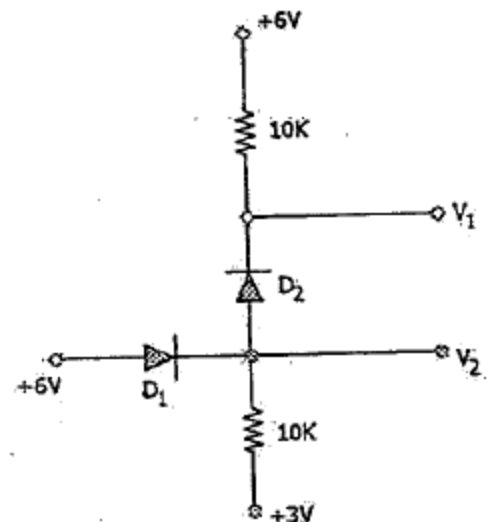
Q6. . The voltages at V_1 and V_2 of the arrangement shown in the figure is (Assume diode drop of 0.6V in forward bias)

- (A)6V and 5.4V (B)5.4V and 6V
 (C)3V and 5.4V (D)6V and 3V



(ISRO-2007)

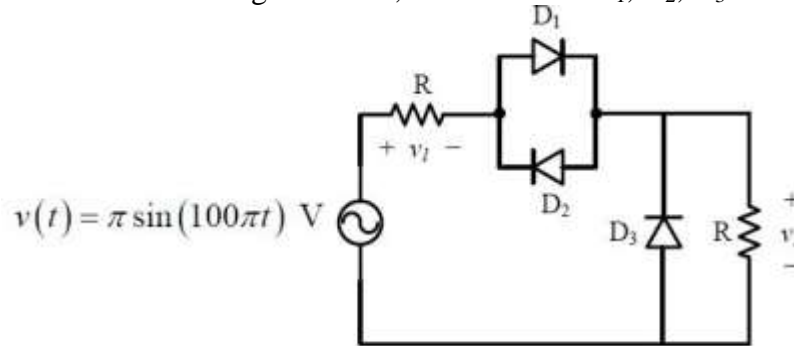Q7. . For the circuit shown in the figure below, assume diode D_1, D_2, D_3 are ideal




Dc component of voltage V_1 and V_2 respectively are

- (A) 0V and 1V (B) -0.5V and 0.5V
(C) 1V and 0.5V (D) 1V and 1V

(GATE-EE-2017-2)

Q8. In the following circuit, the input voltage V_{in} is $100 \sin(100\pi t)$. For $100\pi RC=50$, the average voltage across R (in Volts) under steady-state is nearest to

- (A) 100 (B) 31.8 (C) 200 (D) 63.6

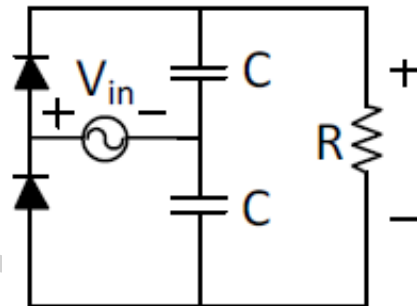

(GATE-EE-2015-2)

Q9. Assuming the diodes to be ideal in the figure, for the output to be clipped, the input voltage v_i must be outside the range